



School of Electrical Engineering and Computer Science
National University of Sciences & Technology (NUST)

Home Assignment No-3

Subject: **Digital Logic Design**

Marks: **50**

Course: **BSCS-10AB**

Issue: **May 02, 2021**

Teacher: **Engr. Arshad Nazir**

Due: **May 09, 2021**

Note:

(10:00 PM)

- ✓ Attempt the given problem set in a sequential order.
- ✓ Make an index showing summary of the problems solved with page numbers and also specify the missing ones.
- ✓ No late submissions will be accepted and the assignments submitted after the due date/time will be graded **zero**.
- ✓ No copying is allowed and assignments found copied will be marked **zero**.
- ✓ The students will submit a certificate with the assignment work stating the originality of their efforts and no copying from others.
- ✓ **Five** marks are reserved for neat and clean work, table of contents, and certificate to be attached with the assignment work.

Problem No-1

Optimize the following Boolean functions together with the don't care conditions d in the forms indicated using map method by finding all the prime implicants and essential prime implicants and apply the selection rule:

- a. $F(W,X,Y,Z) = \pi_M(0,1,6,8,11,12) \cdot \pi_D(3,7,14,15)$ **SOP**
- b. $g = (a' + c + d)(a' + b + e)(a + c' + e')(c + d + e')(b + c + d' + e)(a' + b' + c + e')$ **SOP**
- c. $h(a,b,c,d,e) = \sum_m(1,5,12,13,14,16,17,21,23,24,30,31) + \sum_d(0,2,3,4)$ **POS**
- d. $f(w,x,y,z) = \sum_m(0,1,3,7,8,11,12,13,15)$ **SOP & POS**

Problem No-2

Braille is a system which allows a blind person to read alphanumeric by feeling a pattern of raised dots. Design a circuit that converts BCD to Braille. The table shows the correspondence between BCD and Braille.

A	B	C	D	W X	
				Z	Y
0	0	0	0	.	:
0	0	0	1	.	.
0	0	1	0	:	.
0	0	1	1	.	.
0	1	0	0	.	:
0	1	0	1	.	.
0	1	1	0	:	.
0	1	1	1	:	:
1	0	0	0	.	.
1	0	0	1	.	.

Implement your design with two-level (a) NAND-AND, (b) OR-NAND forms. Assume that double rail inputs are available.

Problem No-3

Implement the following two-level function using multi-level NOR gates:

$$f(x_1, x_2, x_3, x_4, x_5, x_6, x_7) = x_1x_4x_5 + x_1x_4x_6 + x_1x_7 + x_2x_3x_4x_5 + x_2x_3x_4x_6 + x_2x_3x_7$$

Assume that logic gates have a maximum fan in of 2 and the input variables are available in uncomplemented form only.

“Stay Home, Stay Safe”